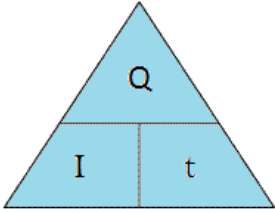
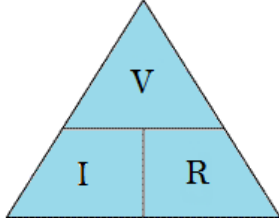
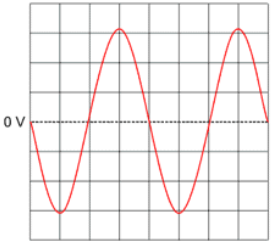
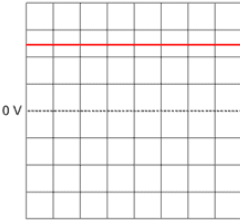
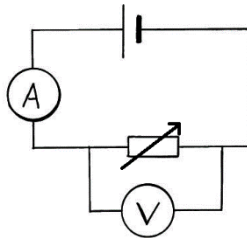
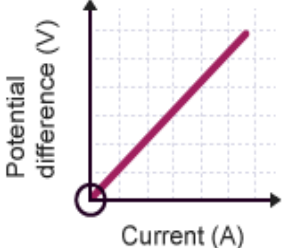
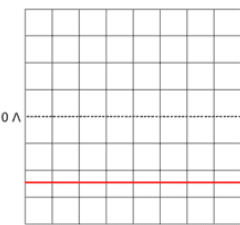
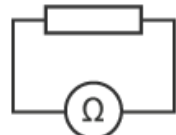
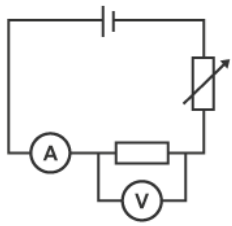
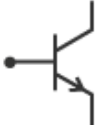



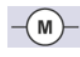





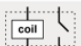
# ELECTRICITY SUMMARY NOTES

<p>Voltage (potential difference) is the energy transferred to each coulomb of charge.</p> <p>It is measured in volts (V).    1 V = 1 J per C</p> <p>Current is the charge transferred per second. It is measured in amps (A). 1A = 1 C per s</p>	<p style="text-align: center;"><b><u>Mains Voltage:</u> 230V, 50 Hz</b></p> <p style="text-align: center;"><b>Factors that <u>increase resistance</u></b></p> <p style="text-align: center;">Increase:</p> <p style="text-align: center;">Temperature</p> <p style="text-align: center;">Length of wire</p> <p style="text-align: center;">Thickness of wire</p>		
<p>charge = current × time</p> <p style="text-align: center;"><math>Q = It</math></p> <div style="text-align: center;">  </div>	<p style="text-align: center;"><b>Voltage = Current x Resistance</b></p> <div style="text-align: center;">  </div> <p style="text-align: center;"><math>V = IR</math></p>		
<p><b><u>A.C. - alternating current</u></b></p> <ul style="list-style-type: none"> <li>- changes direction and magnitude</li> <li>- from the mains</li> </ul> <div style="text-align: center;">  </div>	<p><b><u>D.C. - direct current</u></b> - one direction only</p> <ul style="list-style-type: none"> <li>- from a battery</li> <li>Same magnitude</li> </ul> <div style="text-align: center;">  </div>	<p><b>Ohms Law Experiment</b></p> <p>Adjust resistance of variable resistor and take readings of V &amp; I</p> <div style="text-align: center;">  </div>	<p><b>Ohms Law Graph</b></p> <div style="text-align: center;">  </div>
<p>If the polarity of D.C. trace is reverse (the connections are swapped) the trace goes below the line by the same amount</p>	<div style="text-align: center;">  </div>	<p><b>Resistance opposes the flow of current (Ω)</b></p>	<p>Gradient,  <math>m = V / I = R</math>  <math>m = \frac{y_2 - y_1}{x_2 - x_1}</math></p>
<p><b>Series Rules</b></p> <p><math>I_s = I_1 = I_2 \dots</math></p> <p><math>V_s = V_1 + V_2 \dots</math></p> <p><math>R_T = R_1 + R_2 \dots</math></p> <p>Adding <math>R = R_T</math></p>	<p><b>Parallel Rules</b></p> <p><math>I_s = I_1 + I_2 \dots</math></p> <p><math>V_s = V_1 = V_2 \dots</math></p> <p><math>1/R_T = 1/R_1 + 1/R_2 \dots</math></p>	<p><b>Connecting meters</b></p> <p>Ammeters -&gt; series          Voltmeters -&gt; Parallel</p> <div style="display: flex; align-items: center;"> <div style="text-align: center; margin-right: 20px;">  </div> <div> <p>Ohmmeters -&gt; no power supply</p> </div> </div> <div style="text-align: right; margin-top: 10px;">  </div>	
<p><b>Transistors are electronic switches</b></p>		<p><b>The input voltage controls the switch.</b></p>	
<p><b><u>nnp transistor</u></b>          Input voltage must be <u>0.7V</u></p> <div style="text-align: center; margin-top: 10px;">  </div> <p>or above to switch on the output device.</p>	<p><b><u>n channel enhancement MOSFET</u></b>          Input voltage must be <u>2V</u> or above to switch on the output dev</p> <div style="text-align: center; margin-top: 10px;">  </div>		

## Output Devices


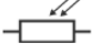
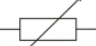
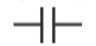
All the components below change electrical energy into another form of energy

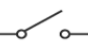

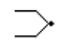

Light Emitting Diode (LED)	Electrical -> Light	
Solenoid	Electrical -> Kinetic	
Motor	Electrical -> Kinetic	

Buzzer	Electrical -> Sound	
Filament Lamp	Electrical -> Light	
Loudspeaker	Electrical -> Sound	
Relay	Electrical -> Kinetic	


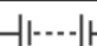

## Input devices

All the components below change another form of energy into electrical energy

Thermistor	T. U. R. D.	
Light Dependant Resistor (LDR)	L. U. R. D.	
Variable Resistor	Resistance can be altered	
Capacitor	Stores charge and energy	

Switch	Completes/breaks circuits	
Microphone	Sound -> Electrical	
Thermocouple	Heat -> Electrical	
Solar Cell	Light -> Electrical	

## Other components

Cell	Provides electrical energy to charges in a circuit	
Battery	Same as cell	
Diode	Allows current to flow in one direction only	



## More about LEDs

Series resistor protects LED from high current

Current flows in opposite direction the arrow

To calculate R:

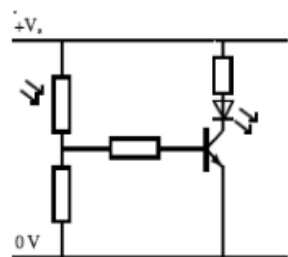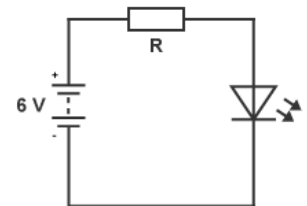
- $V_R = V_S - V_{LED}$
- Use  $R = V_R / I$


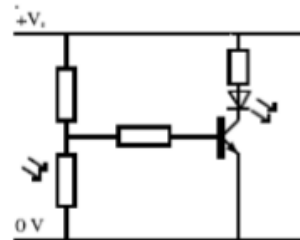
### High Light sensor

Voltage across transistor increases above 0.7V, transistor switches ON LED switches ON


Light  $\uparrow$   $R_{LDR} \downarrow$   $V_{LDR} \downarrow$   $V_R \uparrow$


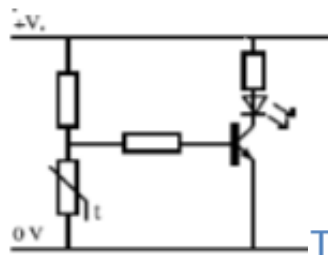
### Low Light sensor

Voltage across transistor increases above 0.7V, transistor switches ON LED switches ON


Light  $\downarrow$   $R_{LDR} \uparrow$   $V_{LDR} \uparrow$


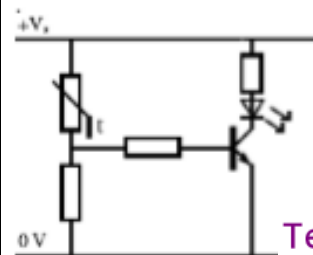
### Switch on Low Temperature

Voltage across transistor increases above 0.7V, transistor switches ON LED switches ON



Temp  $\downarrow$   $R_T \uparrow$   $V_T \uparrow$



### Switch on High Temperature

Voltage across transistor increases above 0.7V, transistor switches ON LED switches ON

Temp  $\uparrow$   $R_T \downarrow$   $V_T \downarrow$   $V_R \uparrow$
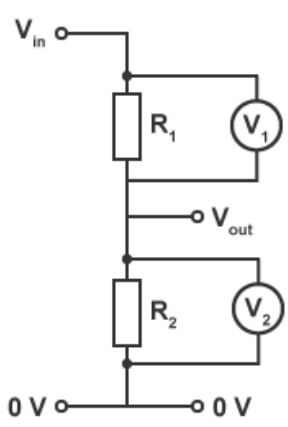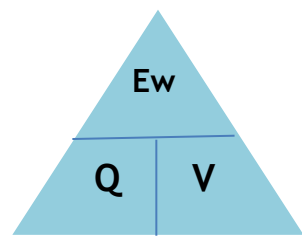
<p><b>Voltage (potential) dividers</b></p> <p>These divide a supply voltage between 2 resistors</p> $\frac{V_1}{V_2} = \frac{R_1}{R_2}$ $V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V_s$ $V_s = V_1 + V_2$		<p>Power is the energy transferred per second</p> <p>It is measured in Watts (W). 1W = 1 J per s</p>	<p><math>E_w = QV</math></p> <p>Energy supplied to the charges</p> <p>= Charge <math>\times</math> voltage</p> 
--	--	--	--


A fuse melts to break the circuit if the current is too high.

Power rating less than 720W – 3A fuse

Power rating above 720W – 13A fuse

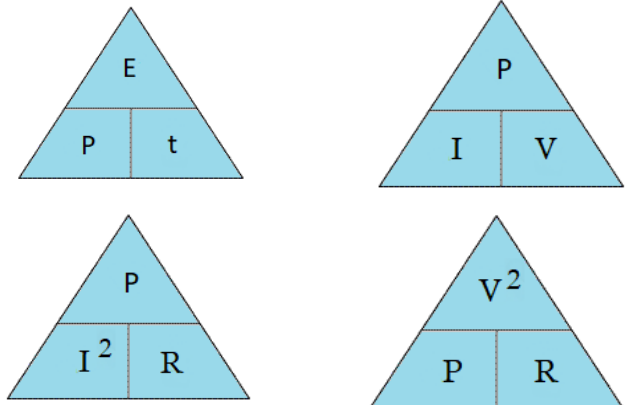
Some appliances with a power rating less than 720W require a 13A fuse as they have a high current on switch on.




<p><b>Power = <math>\frac{\text{Energy}}{\text{Time}}</math></b></p> <p><b>Power = current <math>\times</math> voltage</b> <math>P = IV</math></p> <p><b>Power = current<sup>2</sup> <math>\times</math> resistance</b> <math>P = I^2R</math></p> <p><b>Power = voltage<sup>2</sup> / resistance</b> <math>P = \frac{V^2}{R}</math></p> <p>Greater current/voltage = greater power developed</p>	
--	---

**Charges and Electric fields**



- Opposites ATTRACT

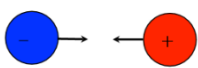

- Like/Similar REPEL

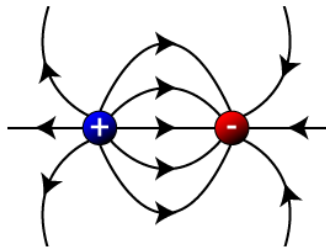

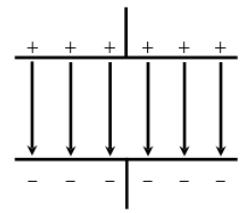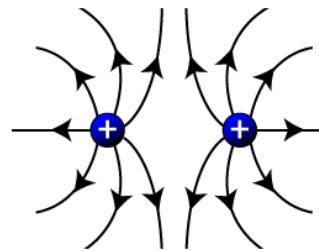A charged particle experiences a force in an electric field



Capacitors store charge on their plates. Capacitance, C, is measured in **farads** (F). Capacitors can be used **with resistors in series as timing devices**.

The bigger the value of the resistance and the bigger the value of the capacitor, the longer it takes to charge to Vs

